

Digital Design
Sequential Circuits II
(Finite State Machines revisited)


March 14, 2002

Finite State Machines

 - **Example: Edge Detector**


Bits are received one at a time (one per cycle),
such as: 000111010 \longrightarrow *time*

Design a circuit that asserts
its output for one cycle when
the input bit stream changes
from 0 to 1.



Try two different solutions.

State Transition Diagram Solution A

 

	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

Solution A, circuit derivation


	IN	PS	NS	OUT
ZERO	0	00	00	0
	1	00	01	0
CHANGE	0	01	00	1
	1	01	11	1
ONE	0	11	00	0
	1	11	11	0

		PS			
		00	01	11	10
IN	0	0	0	0	-
	1	0	1	1	-

$NS_1 = IN \text{ } PS_0$

		PS			
		00	01	11	10
IN	0	0	0	0	-
	1	1	1	1	-

$NS_0 = IN$

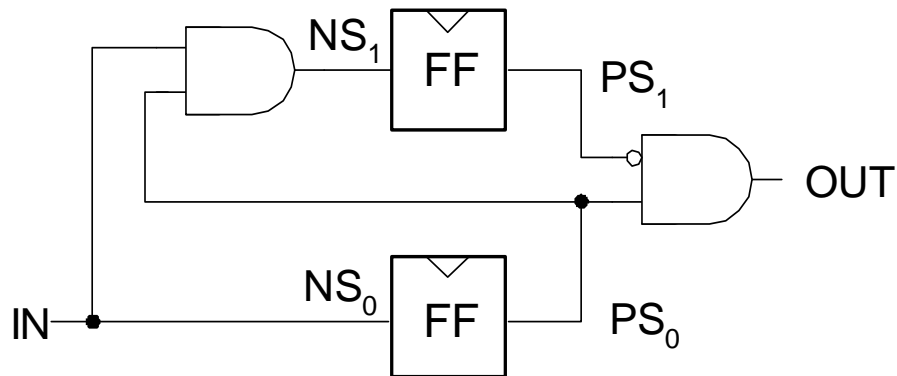


		PS			
		00	01	11	10
IN	0	0	1	0	-
	1	0	1	0	-

$OUT = \overline{PS_1} PS_0$

Solution B

 
Output depends non only on PS but also on input, IN



Let ZERO=0,
ONE=1


IN	PS	NS	OUT
0	0	0	0
0	1	0	0
1	0	1	1
1	1	1	0

NS = IN, OUT = IN PS'

 

What's the *intuition* about this solution?

Edge detector timing diagrams

 

- Solution A: output follows the clock
- Solution B: output changes with input rising edge and is asynchronous wrt the clock.

FSM Comparison

Solution A


Moore Machine

- output function only of PS
- maybe more state
- synchronous outputs
 - no glitching
 - one cycle “delay”
 - full cycle of stable output

Solution B


Mealy Machine

 - output function of both PS & input
- maybe fewer states
- asynchronous outputs
 - if input glitches, so does output
 - output immediately available
 - output may not be stable long enough to be useful:




FSM Recap

Moore Machine

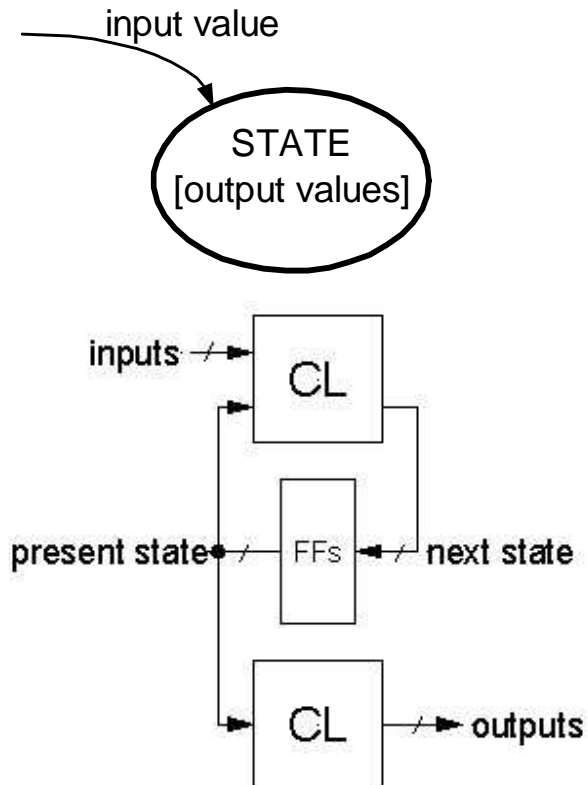

Mealy Machine

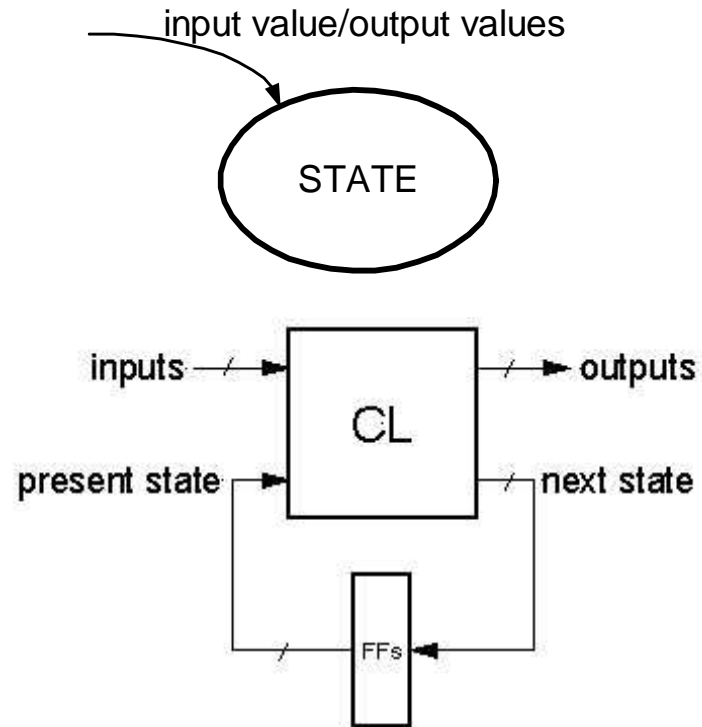

Both machine types allow one-hot implementations.

FSM Optimization

- State Reduction:



Motivation:

lower cost

- fewer flip-flops in one-hot implementations
- possibly fewer flip-flops in encoded implementations
- more don't cares in NS logic
- fewer gates in NS logic

Simpler to design with extra states then reduce later.

  - Example: Odd parity checker.
Two machines - identical behavior.



State Reduction

- State Reduction is based on:

Two states are equivalent if, for each member of the set of inputs, they give exactly the same output and send the circuit either to the same state or to an equivalent state.

If two states are equivalent, one can be eliminated without effecting the behavior of the FSM.

- Several algorithms exist:
 - Row matching method.
 - Implication table method.

- “Row Matching” is based on the state-transition table:


If two states have the same output, *and* both transition to the same next state, *or* both transition to each other, *or* both self-loop, then they are equivalent.

Combine the equivalent states into a new renamed state.

Repeat until no more states are combined.

- Note: This algorithm is slightly different than the book.

Row Matching Example

 

State Transition Table


PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Row Matching Example

PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1


PS	NS		output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

Reduced State Transition Diagram

 

State Reduction

 - The “row matching” method is not guaranteed to result in the optimal solution in all cases, because it only looks at pairs of states.
- For example:



- Another (more complicated) method guarantees the optimal solution:
- **“Implication table”** method:
See Mano, chapter 9.


State Assignment (from Katz)

- In encoded (non-one-hot) FSMs, the choice of binary encodings for the states has an influence on the number of logic gates (or LUTs) needed to compute the next state and outputs.
- For n states, at least s bits are needed for a binary encoding.

$$\text{Where } s = \lceil \log_2 n \rceil$$

- $2^s!$ different encodings exist.
- We will look at several “by-hand” heuristic methods for choosing good assignments.
- Some CAD tools will make assignments automatically.

State Maps

 

Assignment			
State	q2	q1	q0
S0	0	0	0
S1	1	0	1
S2	1	1	1
S3	0	1	0
S4	0	1	1

Assignment			
State	q2	q1	q0
S0	0	0	0
S1	0	0	1
S2	0	1	0
S3	0	1	1
S4	1	1	1


		q1 q0			
		00	01	11	10
q2	0	S0		S4	S3
	1		S1	S2	

		q1 q0			
		00	01	11	10
q2	0	S0	S1	S3	S2
	1			S4	


- “K-maps” are used to help visualize good encodings.
- Adjacent states in the STD should be made adjacent in the map.

State Assignment

 
Alternative heuristics based on input and output behavior as well as transitions:



Highest Priority

 

Medium Priority

 

Lowest Priority

Adjacent assignments to:


states that share a common next state
(group 1's in next state map)

states that share a common ancestor state
(group 1's in next state map)

states that have common output behavior
(group 1's in output map)

Example

Example: 3-bit Sequence Detector

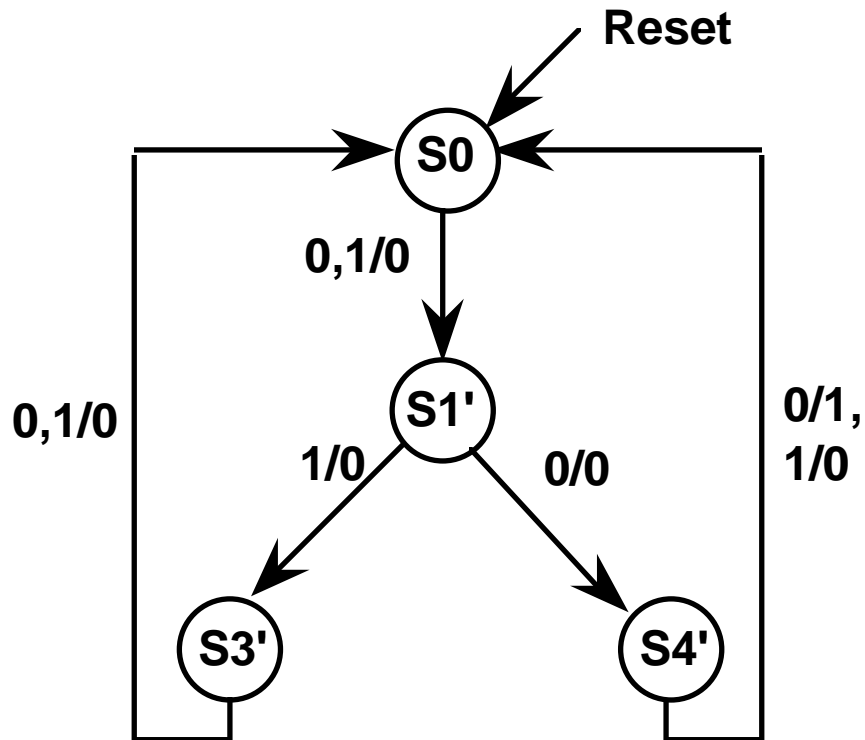

Highest Priority: (S3', S4')

Medium Priority: (S3', S4')

Lowest Priority:

0/0: (S0, S1', S3')

1/0: (S0, S1', S3', S4')

Example

Paper and Pencil Methods

		Q0	
		0	1
Q1	0	S0	S1'
	1	S3'	S4'

		Q0	
		0	1
Q1	0	S0	S3
	1	S1'	S4'


Reset State = 00

Highest Priority Adjacency

Not much difference in these two assignments

State Assignment Example

Another Example: 4 bit String Recognizer

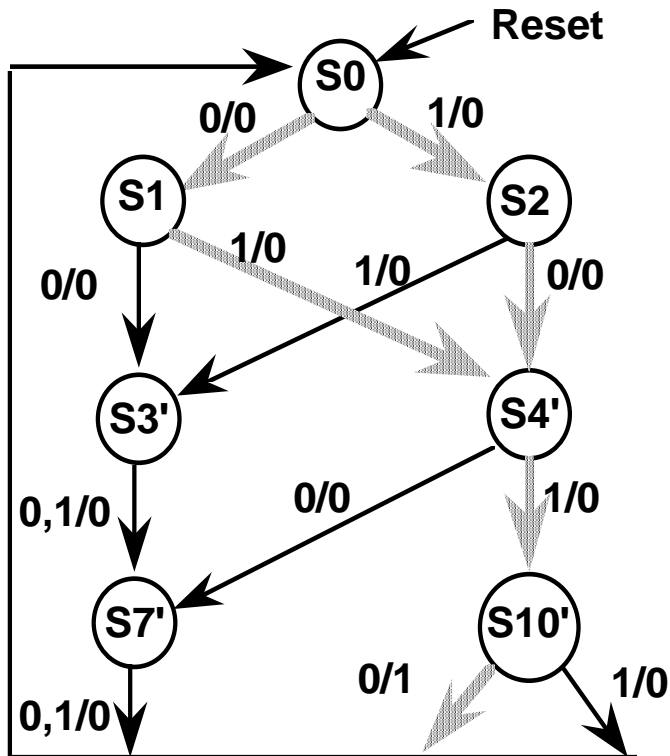

Highest Priority: 2x(S1, S2)
(S3', S4'), (S7', S10')

Medium Priority:
(S1, S2), 2x(S3', S4'), (S7', S10')

Lowest Priority:
0/0: (S0, S1, S2, S3', S4', S7')
1/0: (S0, S1, S2, S3', S4', S7')

State Assignment

State Map

Q1 \ Q0	00	01	11	10
0	S0			
1				

Q1 \ Q0	00	01	11	10
0	S0		S3'	
1			S4'	

Q1 \ Q0	00	01	11	10
0	S0		S3'	S7'
1			S4'	S10'

Q1 \ Q0	00	01	11	10
0	S0	S1	S3'	S7'
1		S2	S4'	S10'

(a)

Q1 \ Q0	00	01	11	10
0	S0			
1				

Q1 \ Q0	00	01	11	10
0	S0			
1	S7'			S10'

Q1 \ Q0	00	01	11	10
0	S0		S3'	
1	S7'		S4'	S10'

Q1 \ Q0	00	01	11	10
0	S0	S1	S3'	
1	S7'	S2	S4'	S10'

(b)

00 = Reset = S0

(S1, S2), (S3', S4'), (S7', S10')
placed adjacently

State Assignment

Effect of Adjacencies on Next State Map

Current State	Next State	
	X = 0	X = 1
(S ₀) 000	001	101
(S ₁) 001	011	111
(S ₂) 101	111	011
(S ₃) 011	010	010
(S ₄) 111	010	110
(S ₇) 010	000	000
(S ₁₀) 110	000	000

Q ₂ Q ₁				
	00	01	11	10
Q ₀ X				
00	0	0	0	X
01	1	0	0	X
11	1	0	1	0
10	0	0	0	1

P₂

Q ₂ Q ₁				
	00	01	11	10
Q ₀ X				
00	0	0	0	X
01	0	0	0	X
11	1	1	1	1
10	1	1	1	1

P₁

Q ₂ Q ₁				
	00	01	11	10
Q ₀ X				
00	1	0	0	X
01	1	0	0	X
11	1	0	0	1
10	1	0	0	1

P₀

Current State	Next State	
	X = 0	X = 1
(S ₀) 000	001	010
(S ₁) 001	011	100
(S ₂) 010	100	011
(S ₃) 011	101	101
(S ₄) 100	101	110
(S ₇) 101	000	000
(S ₁₀) 110	000	000

Q ₂ Q ₁				
	00	01	11	10
Q ₀ X				
00	0	1	0	1
01	0	0	0	1
11	1	1	X	0
10	0	1	X	0

P₂

Q ₂ Q ₁				
	00	01	11	10
Q ₀ X				
00	0	0	0	0
01	1	1	0	1
11	0	0	X	0
10	1	0	X	0

P₁

Q ₂ Q ₁				
	00	01	11	10
Q ₀ X				
00	1	0	0	1
01	0	1	0	0
11	0	1	X	0
10	1	1	X	0

P₀

First encoding exhibits a better clustering of 1's in the next state map